



**LaACES  
Student  
Ballooning  
Course**

# Introduction to Electronics

LaACES, Lecture 02.01



# Electric Potential

1 volt = 1 joule of energy per coulomb of charge

Some examples:

flashlight battery – 1.5 V (DC)

car battery – 12 V (DC)

wall socket – 120 V (AC)

overhead power lines – 6,000 to 250,000 V (AC)



# Electric Current

1 ampere = movement of 1 coulomb of charge per time interval of 1 second

Some examples:

Flashlight – 300 milliamps (DC)

Toaster – 10 amperes (AC)

Automobile starter – 150 amperes (DC)

Quartz wristwatch – a few microamps ( $10^{-6}$  ampere)

Enough to “shock” – a few milliamps ( $10^{-3}$  ampere)



# Electric Resistance

1 ohm ( $\Omega$ ) of resistance allows a potential of 1 volt to cause a current of 1 ampere to flow in a circuit

Ohms's Law  $V = I R$

$V$  = potential in volts

$I$  = current in amperes

$R$  = resistance in oms



# Electric Power

1 watt of power is produced when a potential of 1 volt causes a current of 1 ampere to flow in a circuit

$$P = I V$$

$V$  = potential in volts

$I$  = current in amperes

$R$  = resistance in ohms

$P$  = power in watts

Using Ohm's Law and  $P = I V$ , then  $P = I^2 R = V^2 / R$



# Electric Power

Some examples...

Quartz wristwatch – 0.000001 watt (1 microwatt)

Flashlight – 1 watt

Balloon radio beacon – 5 watts

Table lamp – 60 watts

27" television set – 130 watts

Hair dryer – 1100 watts

Clothes dryer – 5000 watts (5 kilowatts)

State of Louisiana – 8,000,000,000 watts (8000 megawatts)



LaACES  
Student  
Ballooning  
Course

# How To Use a Digital Multimeter

Digital MultiMeter (DMM)

Measures voltage, current, resistance,  
sometimes other parameters

This one cost less than \$5

AC and DC voltage

DC current

Resistance

Diode and Transistor properties

Battery tester





# Taking Measurements (Setup)

BLACK test lead is plugged  
Into the **COM** (common)  
terminal

Select the proper  
**MEASUREMENT** and  
**RANGE** if required

Some DMMs are *autoranging*  
and automatically adjust the  
range







LaACES  
Student  
Ballooning  
Course

# Taking Measurements (Voltage)

RED test lead is plugged  
into the **VΩmA** terminal  
for measuring voltage and  
resistance





LaACES  
Student  
Ballooning  
Course

# Taking Measurements (Current)

Some meters have a common plug for voltage and current, others it is separate

For large DC currents (up to 10 amperes)  
RED test lead is connected  
To the **10ADC** terminal

Current plugs are fused  
(fuses can be blown)






LaACES  
Student  
Ballooning  
Course
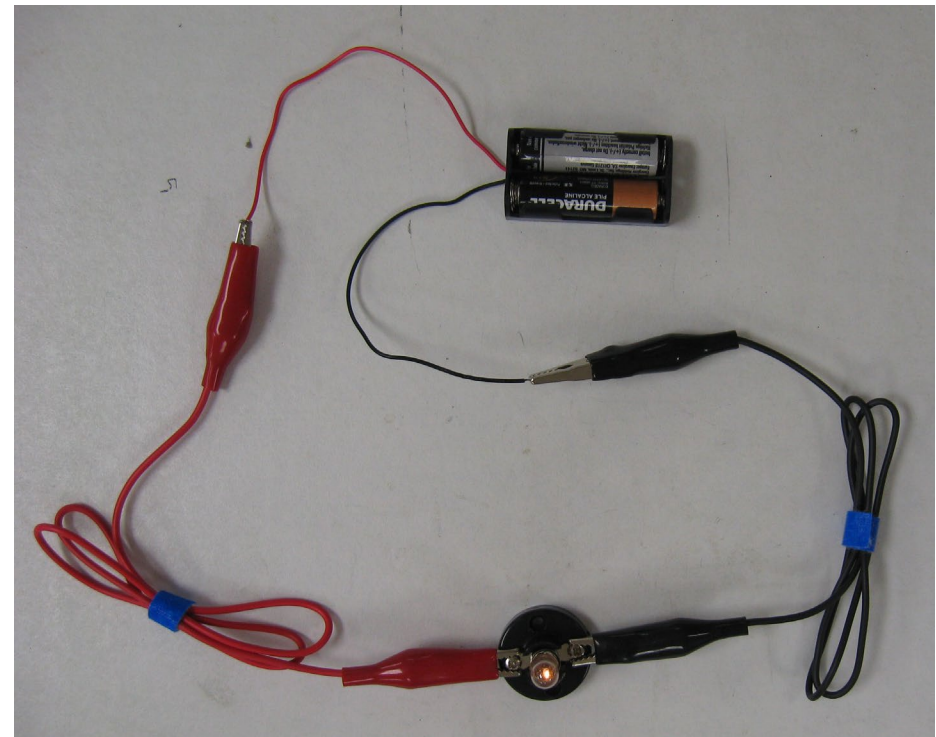
# Voltage Measurement

Here's a simple battery and lamp circuit

Let's measure the voltage across the lamp








# Voltage Measurement

Voltage measurements require the DMM to be connected in *parallel* (*i.e.*, *across*) the circuit element whose voltage is being measured

Note there is a parallel path around the lamp through the multimeter

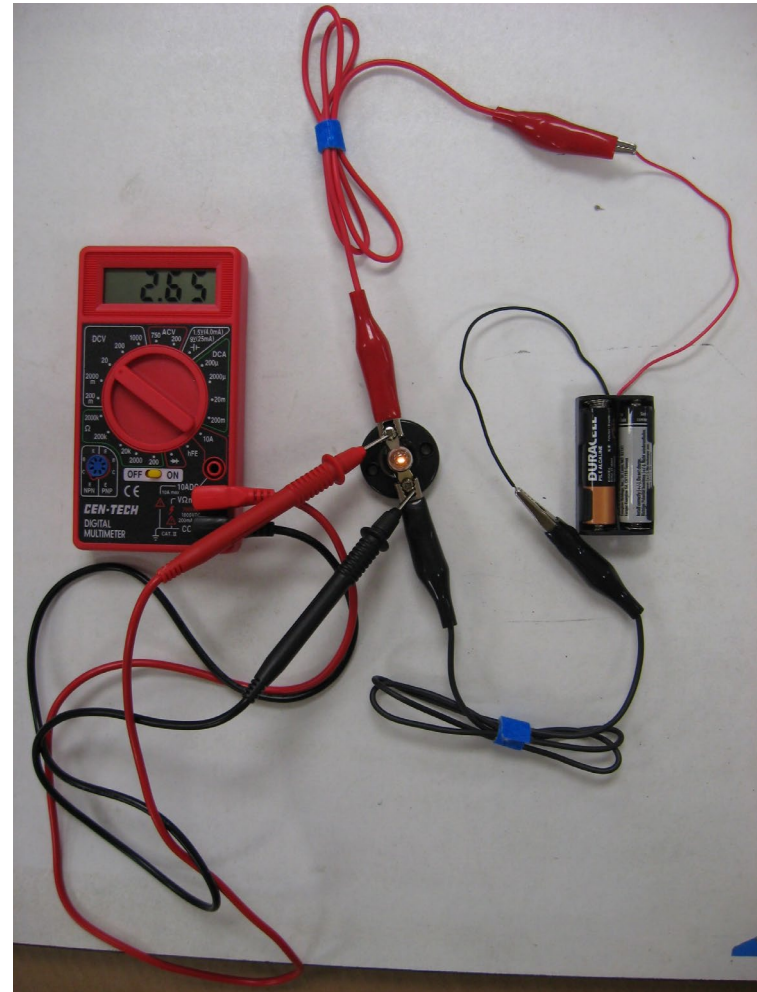In this case the multimeter has a very large resistance so no extra current flows through it






# Current Measurement

To measure current, the DMM must be connected *in series* (i.e., *in line with*) the circuit element whose current is being Measured

The current in the circuit must flow through the meter before getting to the lamp

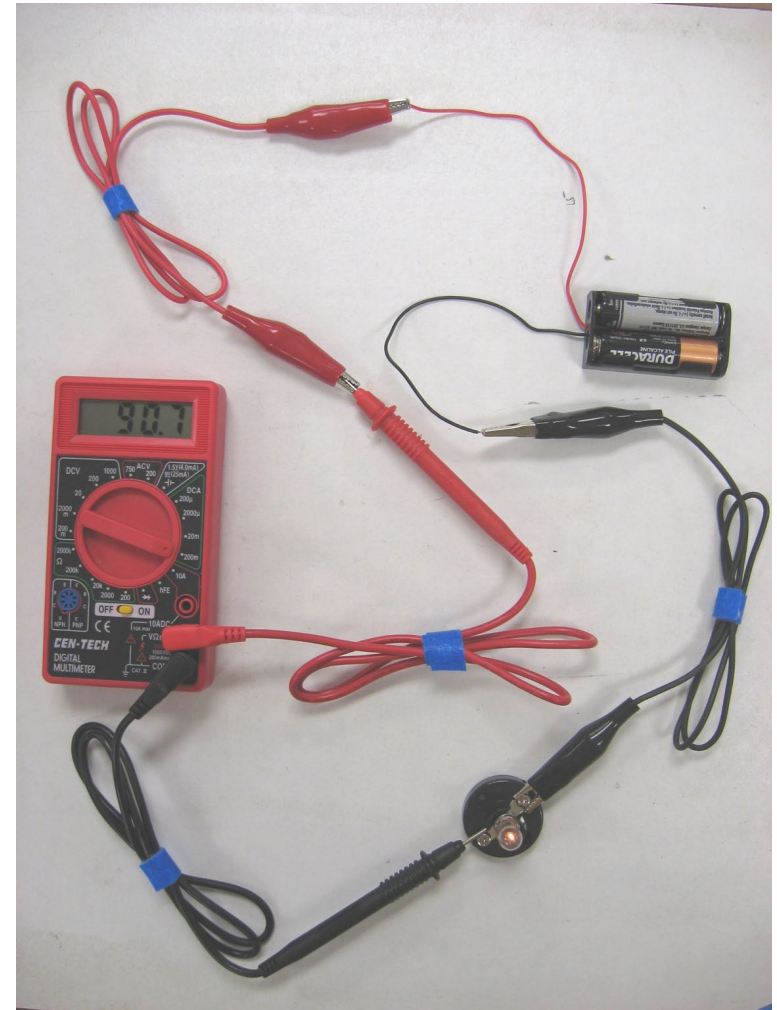The meter has a very low resistance in order not to decrease the current flow






# Resistance Measurement

Here's how to measure the resistance of an element

Note: the element is removed from its circuit

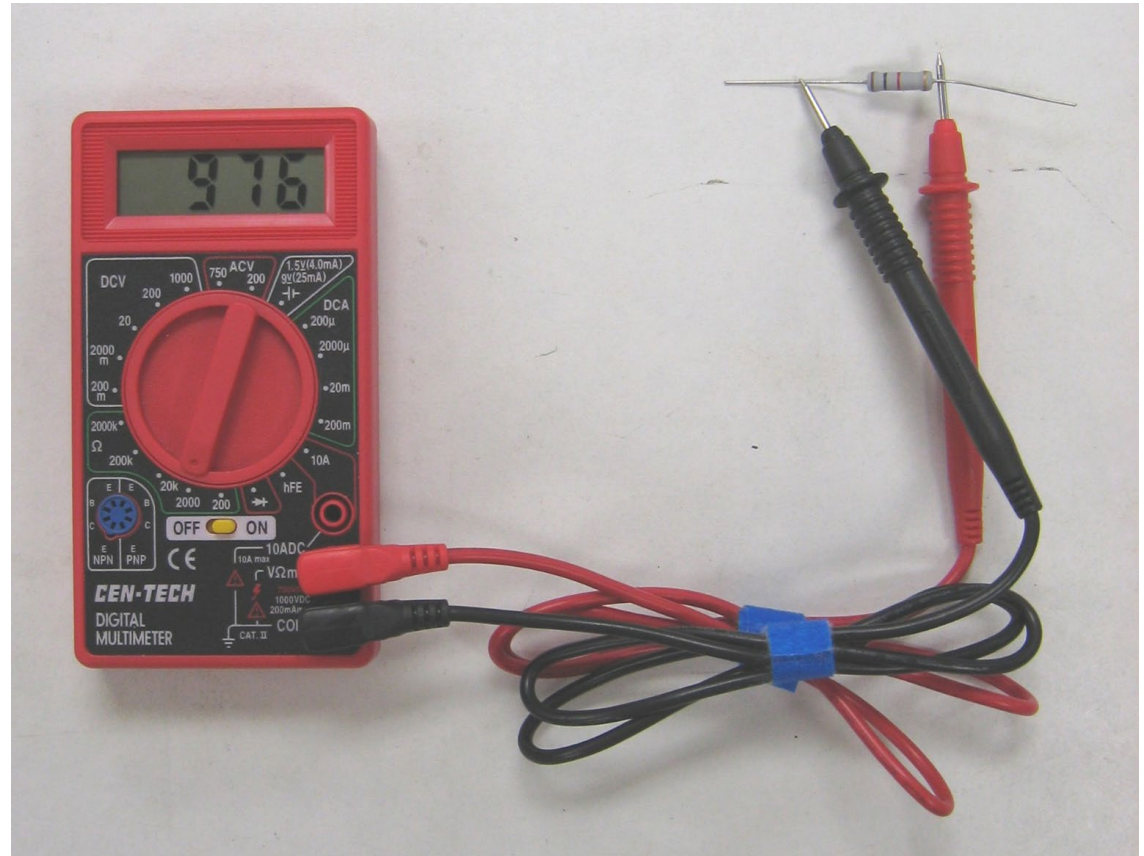If the resistor has power the meter will not be able to accurately measure







# Resistance Measurement

The RANGE is 0-2000  $\Omega$  So the reading is interpreted as 976  $\Omega$ , or 0.976 K  $\Omega$

If the meter was on the 20k setting the meter would read 0.976 instead





**LaACES  
Student  
Ballooning  
Course**

**\*\*\*\*\*WARNING\*\*\*\*\***

**Don't try this at home.**





# LaACES Student Ballooning Course

What happens if you connect a DMM, *set to read current*, in parallel with a voltage source, such as a battery?

Some  $V$  small  $R$  means large  $I$

Some of the magic smoke may  
Escape from your DMM. (You may  
damage your circuit or meter)

Fortunately, even this inexpensive  
DMM includes a protective fuse.  
So your DMM **might** not be destroyed.





**LaACES  
Student  
Ballooning  
Course**

