



**LaACES
Student
Ballooning
Course**

Lecture 02.01

Introduction to Electronics



Electric Potential

1 volt = 1 joule of energy per coulomb of charge

Some examples:

flashlight battery – 1.5 V (DC)

car battery – 12 V (DC)

wall socket – 120 V (AC)

overhead power lines – 6,000 to 250,000 V (AC)



Electric Current

1 ampere = movement of 1 coulomb of charge per time interval of 1 second

Some examples:

Flashlight – 300 milliamps (DC)

Toaster – 10 amperes (AC)

Automobile starter – 150 amperes (DC)

Quartz wristwatch – a few microamps (10^{-6} ampere)

Enough to “shock” – a few milliamps (10^{-3} ampere)



Electric Resistance

1 ohm (Ω) of resistance allows a potential of 1 volt to cause a current of 1 ampere to flow in a circuit

Ohms's Law $V = I R$

V = potential in volts

I = current in amperes

R = resistance in oms



Electric Power

1 watt of power is produced when a potential of 1 volt causes a current of 1 ampere to flow in a circuit

$$P = I V$$

V = potential in volts

I = current in amperes

R = resistance in ohms

P = power in watts

Using Ohm's Law and $P = I V$, then $P = I^2 R = V^2 / R$



Electric Power

Some examples...

Quartz wristwatch – 0.000001 watt (1 microwatt)

Flashlight – 1 watt

Balloon radio beacon – 5 watts

Table lamp – 60 watts

27" television set – 130 watts

Hair dryer – 1100 watts

Clothes dryer – 5000 watts (5 kilowatts)

State of Louisiana – 8,000,000,000 watts (8000 megawatts)



How To Use a Digital Multimeter

Digital MultiMeter (DMM)

Measures voltage, current, resistance,
sometimes other parameters

This one cost less than \$5

AC and DC voltage

DC current

Resistance

Diode and Transistor properties

Battery tester





Taking Measurements (Setup)

BLACK test lead is plugged
Into the **COM** (common)
terminal

Select the proper
MEASUREMENT and
RANGE if required

Some DMMs are *autoranging*
and automatically adjust the
range





LaACES
Student
Ballooning
Course

Taking Measurements (Voltage)

RED test lead is plugged into the **VΩmA** terminal for measuring voltage and resistance





Taking Measurements (Current)

Some meters have a common plug for voltage and current, others it is separate

For large DC currents
(up to 10 amperes)

RED test lead is connected
To the **10ADC** terminal

Current plugs are fused (fuses can be blown)






LaACES
Student
Ballooning
Course

Voltage Measurement

Here's a simple battery
and lamp circuit

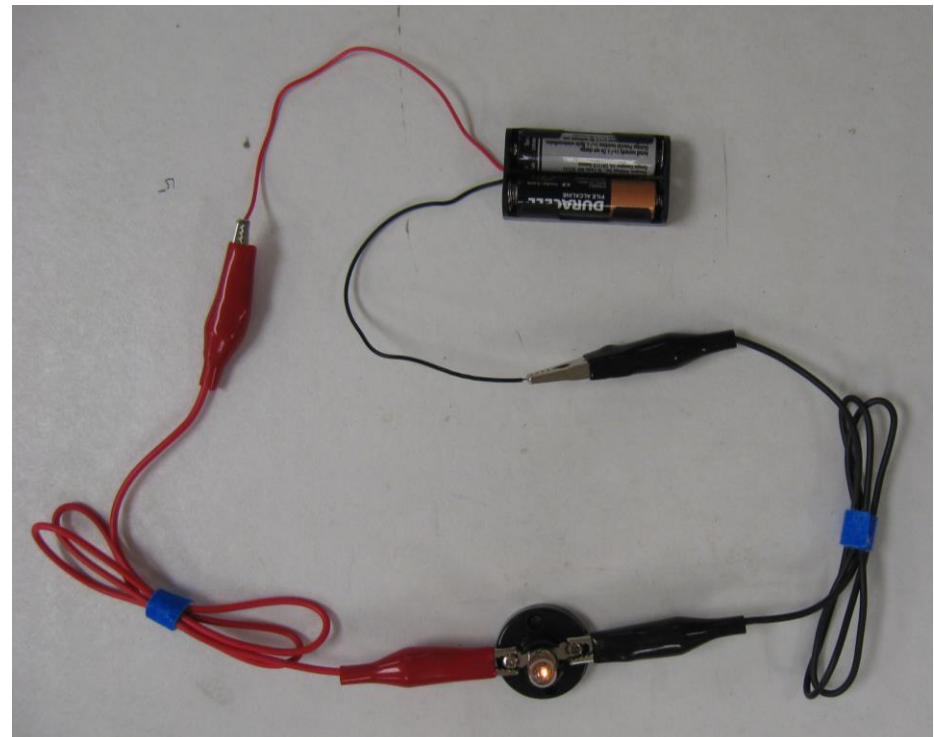Let's measure the voltage
across the lamp






Voltage Measurement

Voltage measurements require the DMM to be connected in *parallel* (*i.e.*, *across*) the circuit element whose voltage is being measured

Note there is a parallel path around the lamp through the multimeter

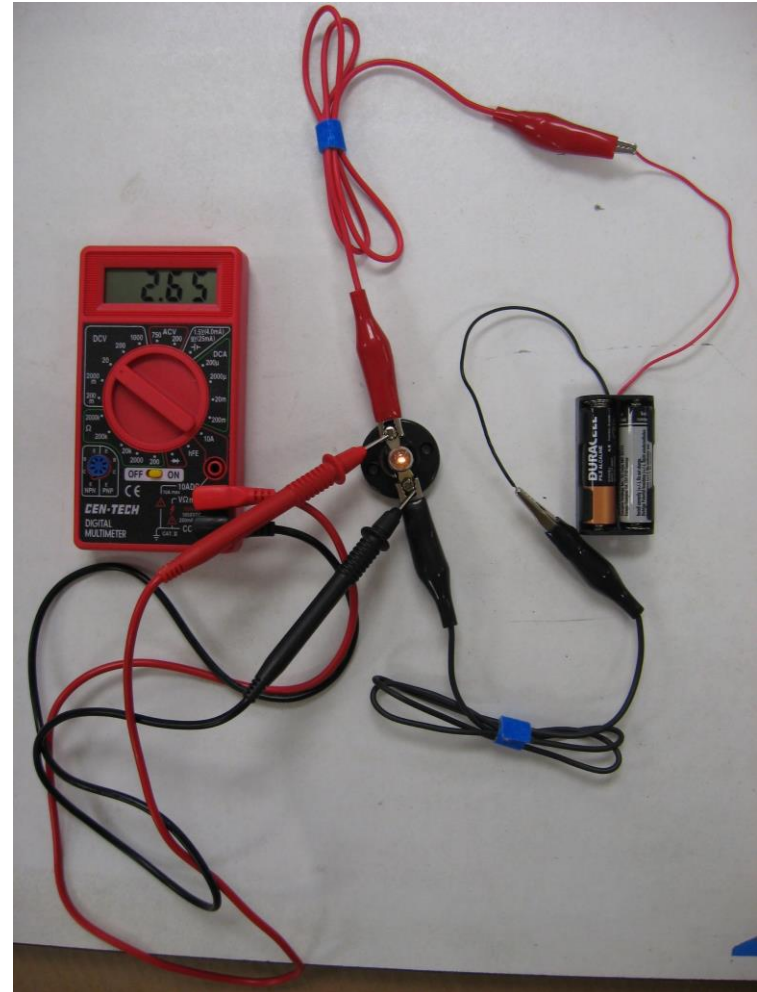In this case the multimeter has a very large resistance so no extra current flows through it






Current Measurement

To measure current, the DMM must be connected *in series* (i.e., *in line with*) the circuit element whose current is being Measured

The current in the circuit must flow through the meter before getting to the lamp

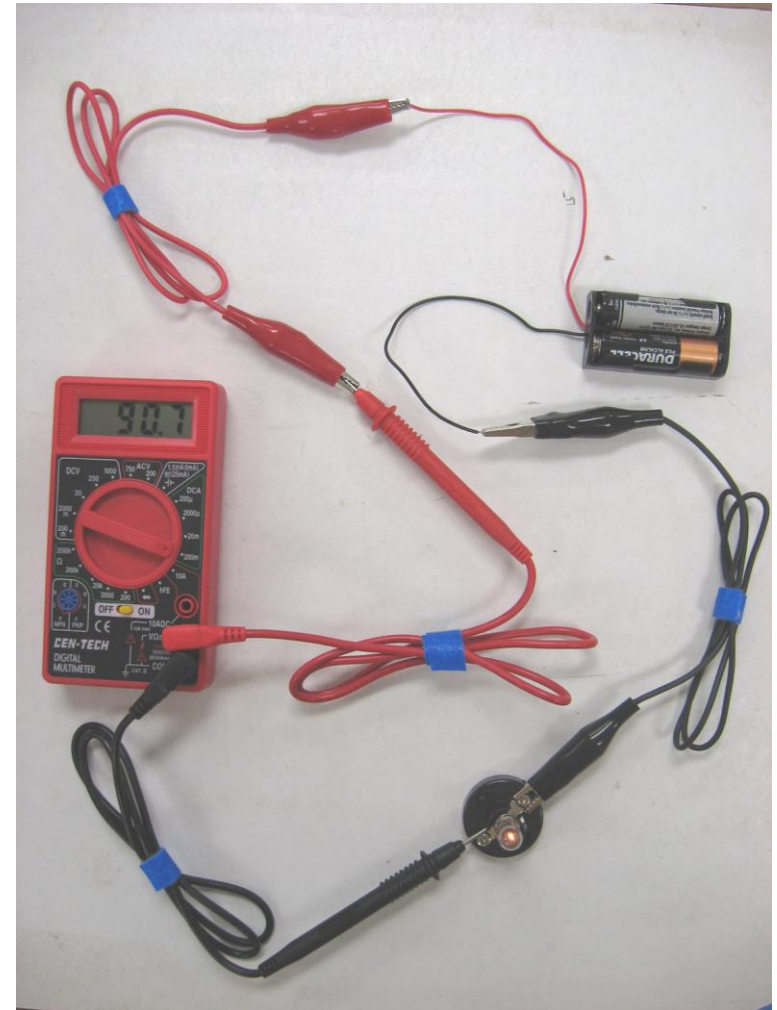The meter has a very low resistance in order not to decrease the current flow






Resistance Measurement

Here's how to measure the resistance of an element

Note: the element is removed from its circuit

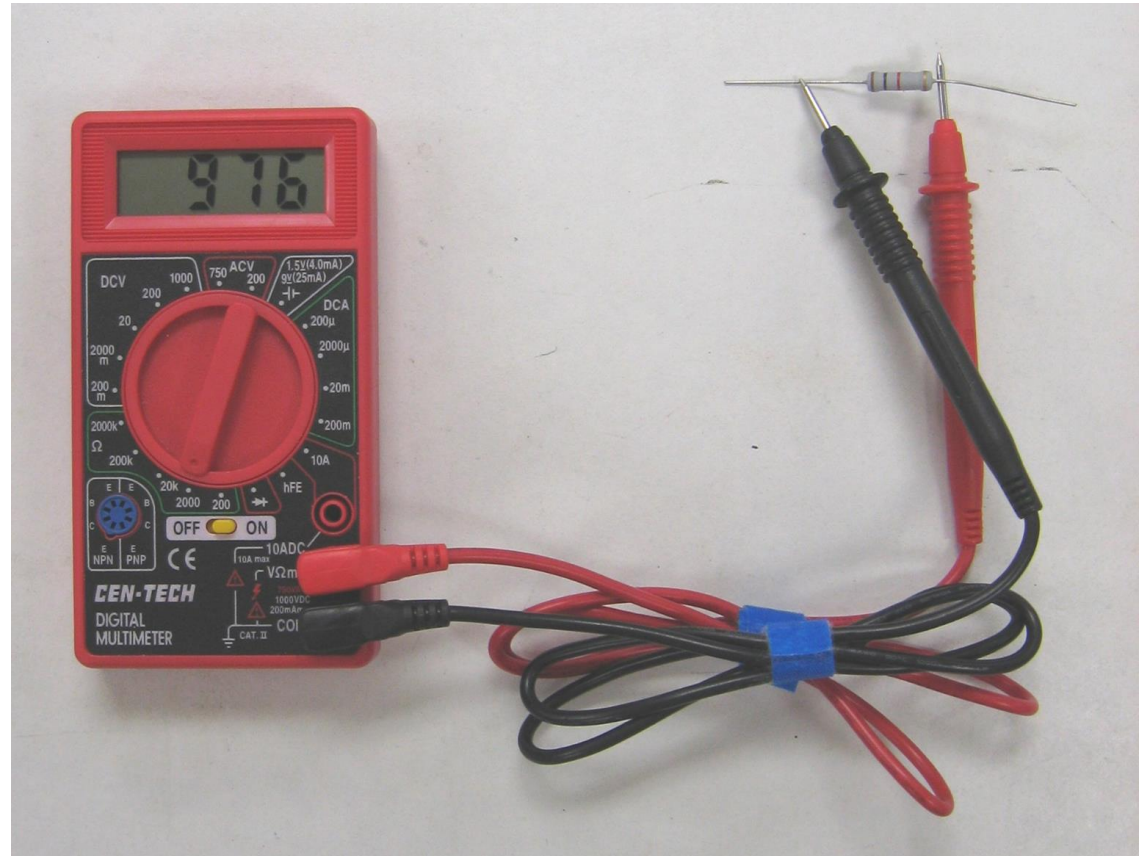If the resistor has power the meter will not be able to accurately measure





LaACES
Student
Ballooning
Course

Resistance Measurement

The RANGE is 0-2000 Ω So the reading is interpreted as 976 Ω , or 0.976 K Ω

If the meter was on the 20k setting the meter would read 0.976 instead





**LaACES
Student
Ballooning
Course**

*******WARNING*******

Don't try this at home.



LaACES Student Ballooning Course

What happens if you connect a DMM, *set to read current*, in parallel with a voltage source, such as a battery?

Some V small R means large I

Some of the magic smoke may Escape from your DMM. (You may damage your circuit or meter)

Fortunately, even this inexpensive DMM includes a protective fuse. So your DMM **might** not be destroyed.





**LaACES
Student
Ballooning
Course**

