







**LaACES
Student
Ballooning
Course**

Lecture L02.03

The Operational Amplifier



Amplification and Attenuation

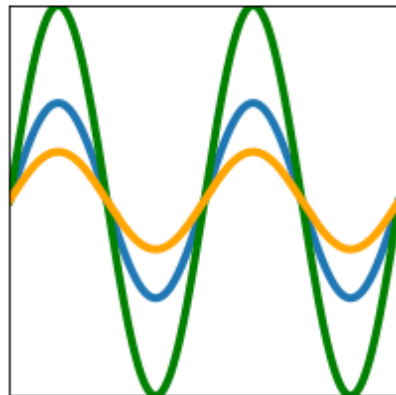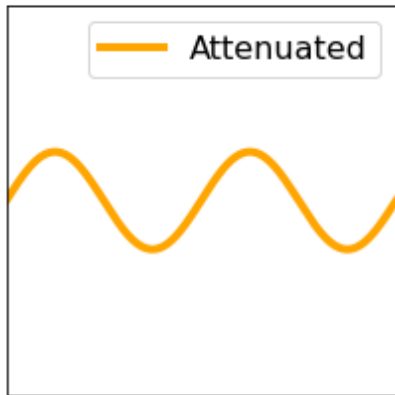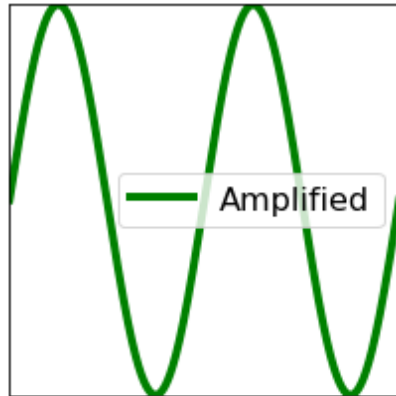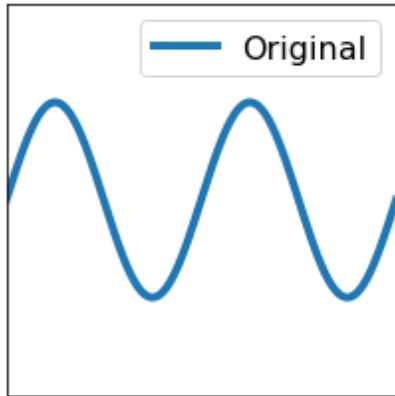

When a signal is too small to be measured correctly, the signal can be amplified.

Amplification is the process of increasing the amplitude of an electrical signal. (Gain >1)

Sometimes, a signal is strong enough to damage equipment or other devices or exceed the desired thresholds.

Attenuation is the process of reducing the power of an electrical sensor. (Gain $0-1$)


Attenuation can occur when a signal is sent over long distances.



Signal Conditioning Circuit

Operational Amplifier or “Op amp”

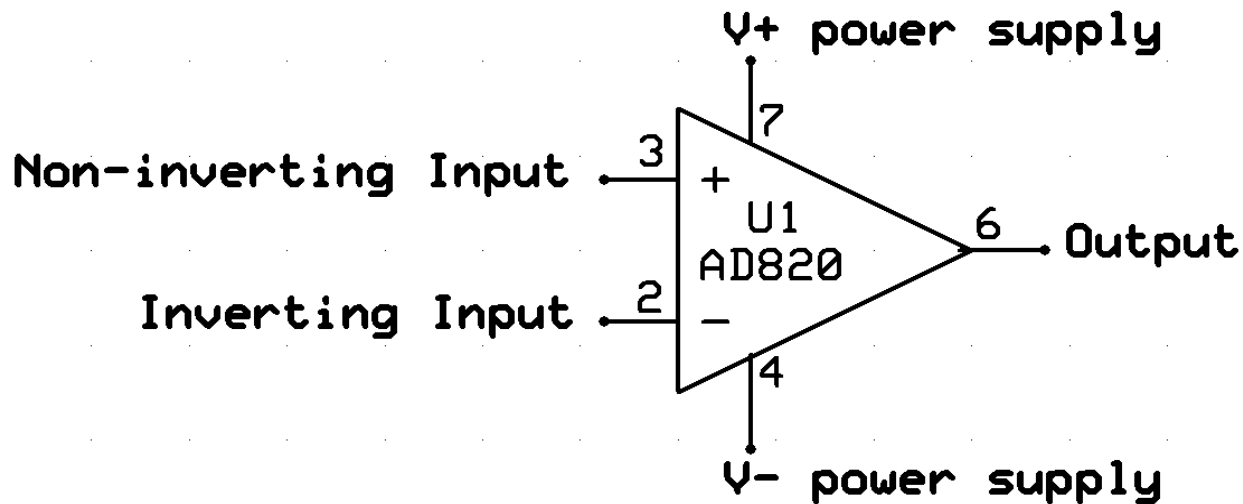
Amplifying circuits are built using an IC called an op amp.





Op Amp Connections - Power

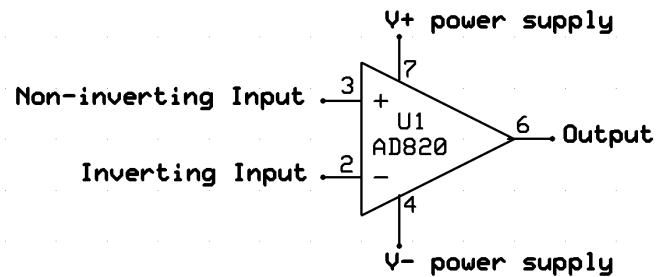
- $V_{\text{supply}+}$ (often called V_{cc})
 - Maximum output voltage will be slightly lower than this voltage
- $V_{\text{supply}-}$
 - Maybe 0V or GND, can often be negative
 - Minimum output voltage will be slightly higher than this voltage
- Current at the output will be drawn via these connections





Op Amp Connections - Inputs

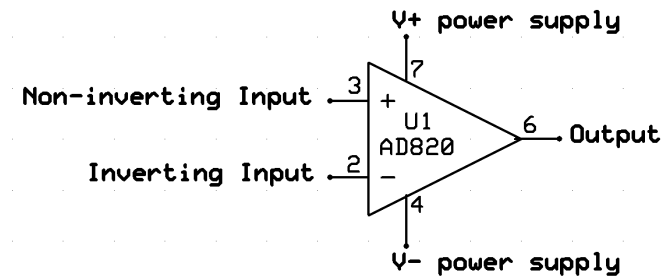
- V_{in+} ($V+$)
 - Non-inverting input
 - Input used when do not want to switch signal to negative
- V_{in-}
 - Inverting input
 - Used when switching signal sign is desired
 - Also used to for creating an offset or subtracting two signals
- The input signal designated V_{in} will be connected to one of these pins





Op Amp Connections - Output

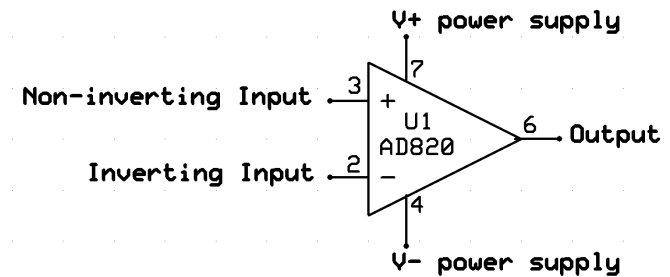- V_{out}
 - The circuit will be designed to change this
 - Will be connected back to one of the inputs to create a feedback loop
 - Op Amp will vary V_{out} to satisfy the **Golden Rules**
 - Limited between V_{s+} and V_{s-}





Transfer Function

The equation of between the input and the output of the amplifier is called the **transfer function**.


Usually, the transfer function is linear (at least over range)

The slope is the **gain** and the intercept the **offset**.

In the plot to the left we are amplifying a small (0.450-0.800 V) signal to 0-3V

$$\text{Gain} = 8.571$$

$$\text{Offset} = -3.857 \text{ V}$$

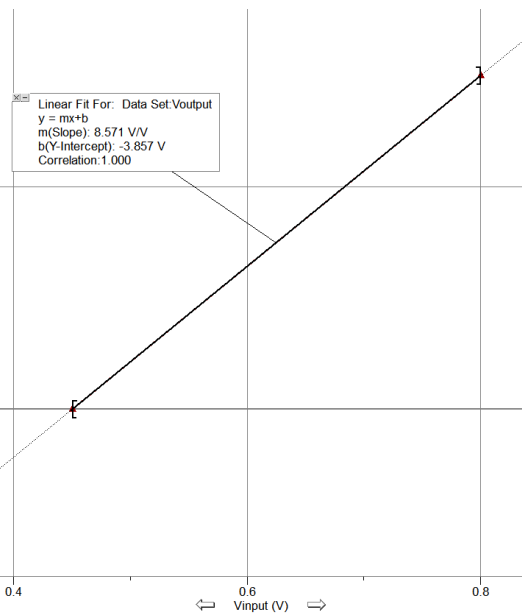



Op Amp Golden Rules

If V_{out} is connected to one of the inputs forming a feedback loop, V_{out} will vary to satisfy the following rules:

- I. The output changes to make the voltage difference between both inputs zero.
($V_+ = V_-$)**

- II. The inputs draw no current. ($I_+ = I_- = 0A$)**



Signal Conditioning Circuit


Example 1: Buffer

No resistors so the equations are simple

$$V_{in} = V_{+}$$

$$V_{+} = V_{-} \text{ (Golden Rule)}$$
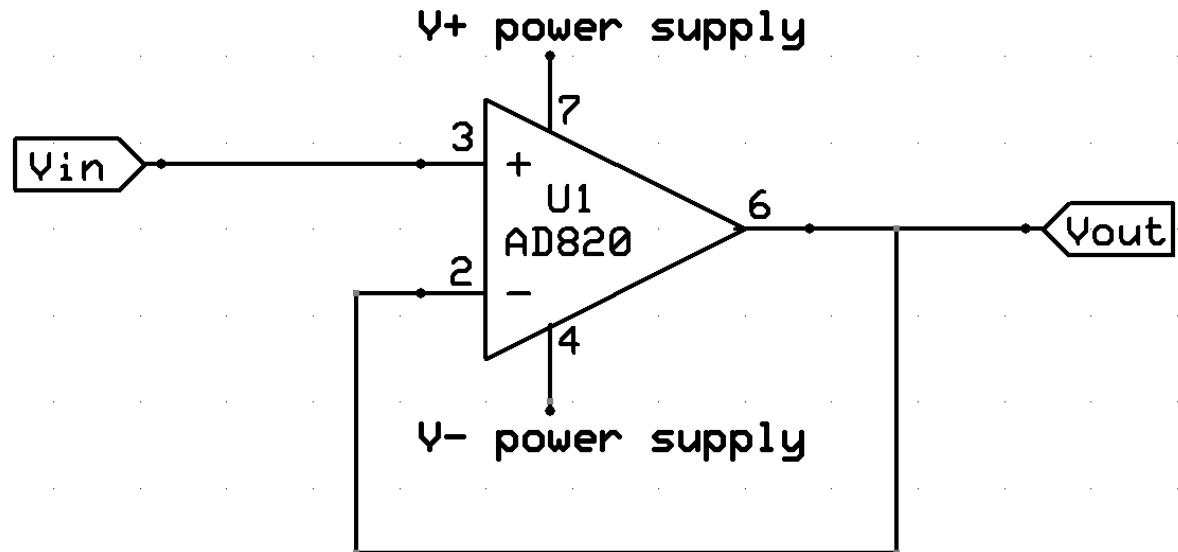
$$V_{-} = V_{out} \quad \text{Therefore } V_{in} = V_{out}$$






Signal Conditioning Circuit

Buffer usage

A buffer provides voltage or current isolation between to components to prevent the signal from affecting the performance of a component.

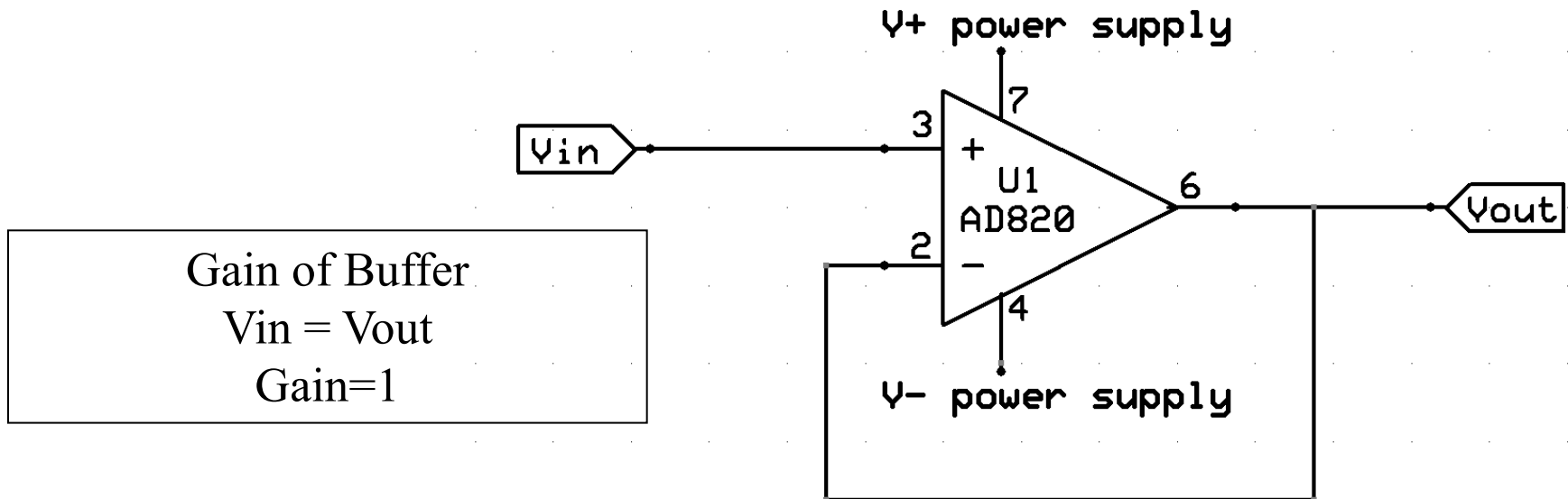Current on V_{out} comes from the supply, not V_{in} .





Signal Conditioning Circuit

Non-Inverting Amplifier Example


Now we have some resistors and possible current paths so things are more complicated.

$V_{in} = V_{+} = V_{-}$ (Golden Rule)

Since no current can go into V_{-} we know all the current through R_{fb} has to go through R_{in} . Using Ohms Law ($I = V/R$), we can write that out as:

$$\frac{V_{out} - V_{-}}{R_{fb}} = \frac{V_{-} - 0V}{R_{in}}$$

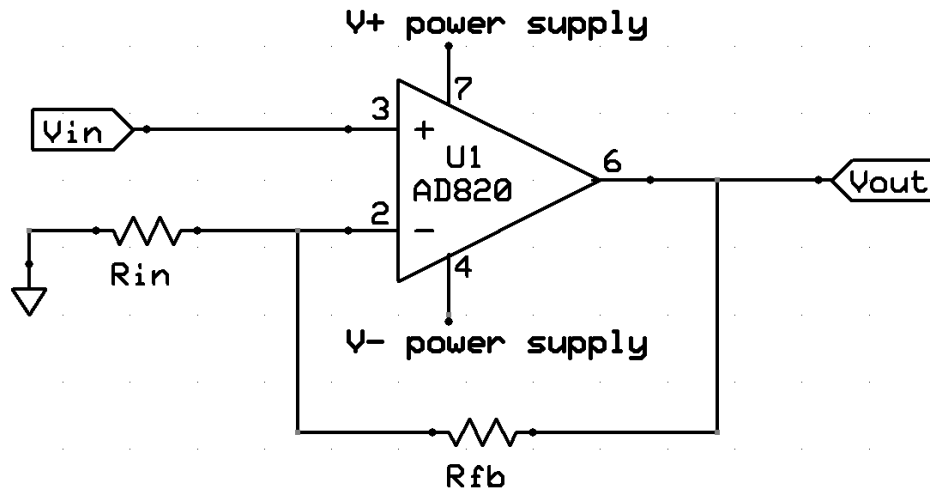But since $V_{-} = V_{in}$ we can
Substitute and solve for V_{out}





Signal Conditioning Circuit


Non-Inverting Amplifier Usage

Non-inverted op amps have V_{in} connected to the positive terminal. This is commonly used in electronics to amplify DC signal.

$$V_{out} = V_{in} \left[1 + \frac{R_{fb}}{R_{in}} \right]$$

$$G = 1 + \frac{R_{fb}}{R_{in}}$$

Gain > 0

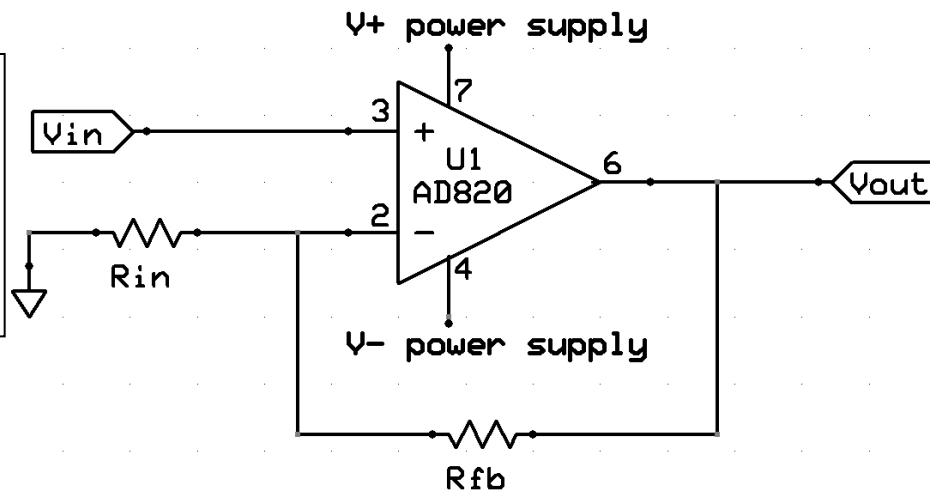



Signal Conditioning Circuit


Inverting Amplifier

Inverted op amps have V_{in} connected to the negative terminal.

Signal is inverted (flipped).

$$V_{out} = -V_{in} \left[\frac{R_{fb}}{R_{in}} \right]$$

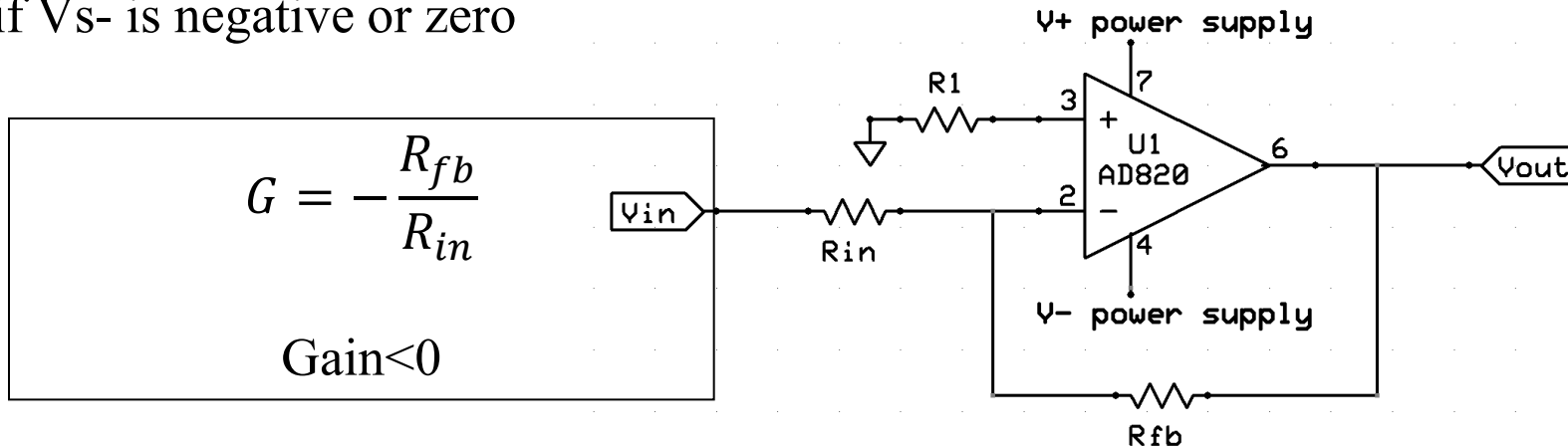Note: the gain is negative so it is important to consider the sign of V_{in} and if V_{s-} is negative or zero






Signal Conditioning Circuit

Summing Amplifier
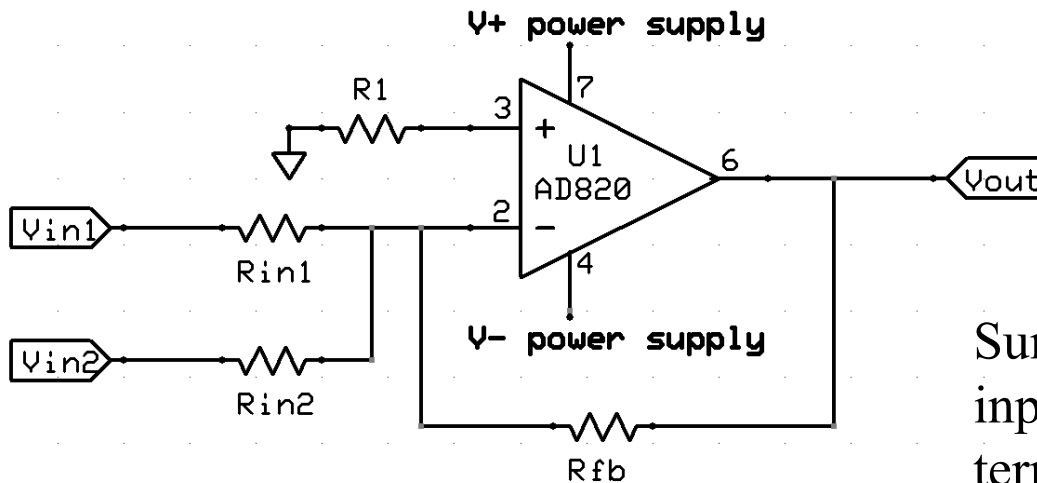
$$V_{out} = -\left[V_{in1} \frac{R_{fb}}{R_{in1}} + V_{in2} \frac{R_{fb}}{R_{in2}}\right]$$




Summing op amps have multiple inputs are connected into a single terminal. Can be inverting (shown here) or noninverting.



Signal Conditioning Circuit

Difference Amplifier
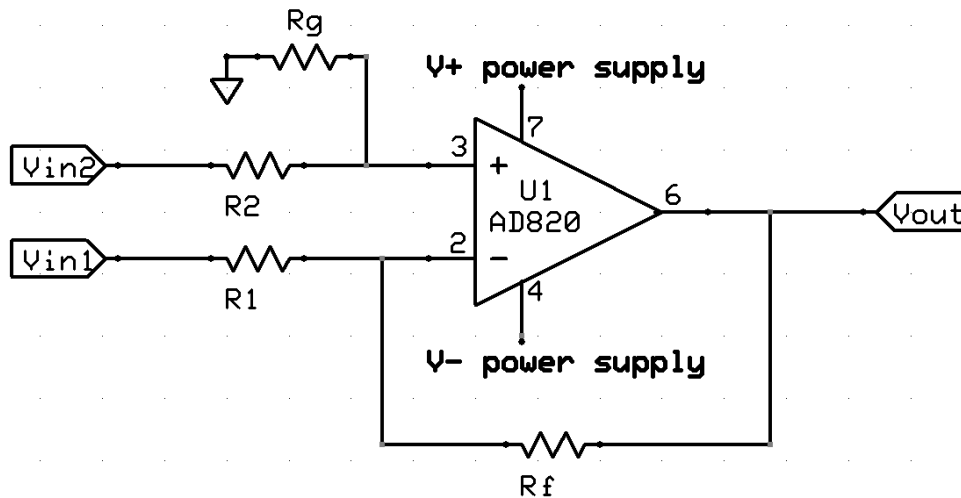
$$V_{out} = (V_{in2} - V_{in1}) \left(\frac{R_f}{R_1} \right) \quad \text{if } \frac{R_f}{R_1} = \frac{R_g}{R_2}$$





A difference op amp has an input into both the negative and positive terminals.

It amplifies the difference between the two signals.

Operational Amplifier ICs

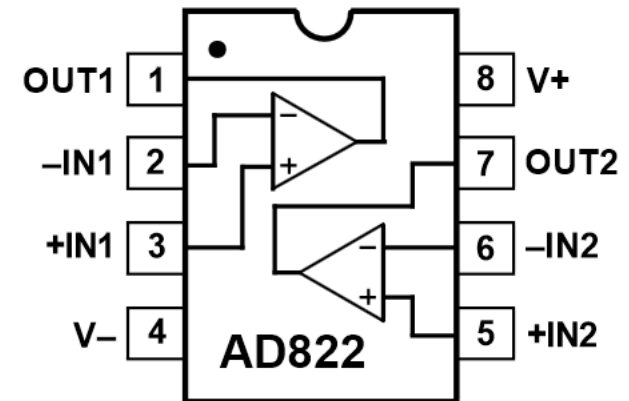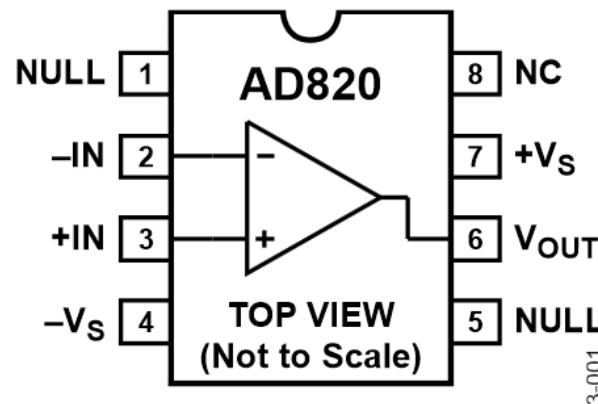Available in Single(1x), Dual(2x), Quad(4x) Packages
 May be Bipolar power supply (ex. $\pm V_s = \pm 12V$)
 Single supply operation (ex. +12V, GND)
 Variety of voltage and frequency ranges for different chips.





Other Types of Amplifying Circuits

- A common variation is to add an offset to previous examples, which shifts the entire signal by a constant amount up and down.
- By adding capacitors and or inductors you can make the gain of a circuit depend on a frequency, this allows you to filter undesirable signals (like high frequency RF noise) out
- It is also common to have multiple stages of amplification; using a buffer to isolate an amplified signal from the rest of the circuit.