



Basic Digital I/O




Digital vs Analog Signal



- I/O stands for “input & output,” This is how we will communicate information to and from the microcontroller
- Digital means that it comes in a discrete set of possible values
 - For the Arduino (and most microcontrollers), these are 0 and 1
- This is opposed to an analog signal, which can take any possible value within some range
- IF you look at a signal as it varies with time
 - Analog will be a smooth continuous wave
 - Digital will be a series of square pulses with sharp, sudden changes

Analog Signal

 

Digital Signal



Characteristics of a Digital Signal



To use digital signals as input or output we need to specify some details


- How is the signal being transmitted?
 - What is a physical connection?
 - Is it a voltage, current, infrared light?
- What defines 1 and what is a 0?
 - These are logic levels, for the Arduino these are based on voltage
- What do the 1s and 0s mean
 - For anything other than a single, simple On/Off you need to define some kind of communication protocol



Logic Levels Defining 0 and 1



- The manufacturer of a digital device will give a set of specifications that define the voltages for High(0) and Low (0)
- These are called the “Logic Levels”
 - When discussing, you will often see terms like 5V TTL or 3.3V CMOS
 - This is the underlying technology (ex., TTL - Transistor to Transistor Logic) and nominal voltage level
- Devices will further group devices into “Logic Families” that share logic levels and additional specs
 - For example, HCT uses the TTL levels but has additional high-speed capabilities

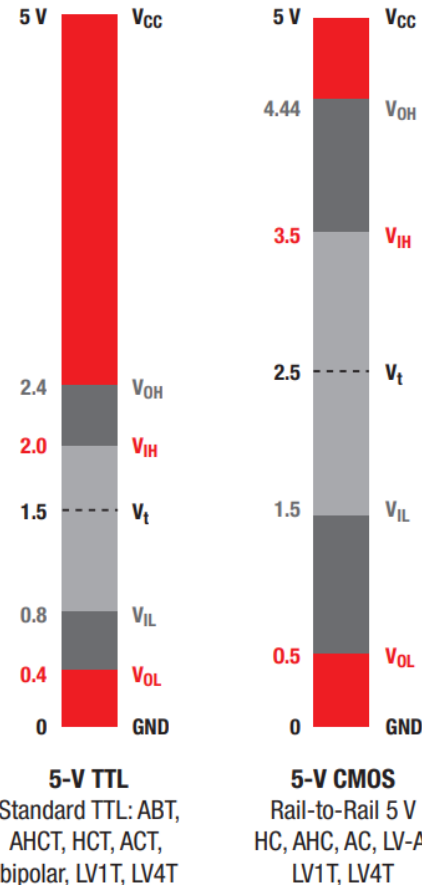


5V TTL and CMOS Logic levels for TI Devices
<https://www.ti.com/lit/sg/sdyu001ab/sdyu001ab.pdf?ts=1758714419432>



Logic Levels Output



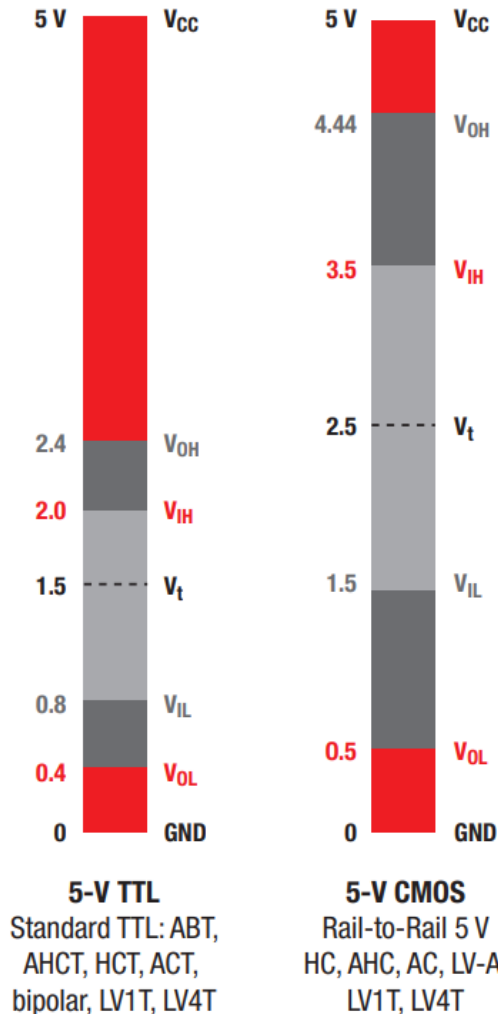- V_{OH} (**V**oltage **O**utput **H**igh) - Minimum voltage that will be seen when the output is high
 - So a digital 1 output will be between V_{OH} and V_{CC}
- V_{OL} (**V**oltage **O**utput **L**ow) - Maximum voltage that will be seen when the output is low
 - So a digital 0 output will be between 0 and V_{OL}







Logic Levels Input



 - V_{IH} (**V**oltage **I**nput **H**igh) - Minimum voltage that will be considered high
 - Any voltage between V_{IH} and V_{CC} will be read as a 1
- V_{IL} (**V**oltage **I**nput **L**ow) - Maximum voltage that will be considered a low
 - Any voltage between 0 and V_{IL} will be read as a 0



 5-V TTL
Standard TTL: ABT, AHCT, HCT, ACT, bipolar, LV1T, LV4T




5-V CMOS
Rail-to-Rail 5 V HC, AHC, AC, LV-A, LV1T, LV4T



Intermediate Region



 - Notice the gap between V_{IH} and V_{IL} ? Because of this gap, there is a sharp distinction between 0 and 1
- This makes digital signals less susceptible to errors caused by “background noise,” which would normally affect an analog signal
- Also notice the outputs are more restricted than the inputs, this allows for slight voltage drop or rise between the output and input



5-V TTL
Standard TTL: ABT, AHCT, HCT, ACT, bipolar, LV1T, LV4T


5-V CMOS
Rail-to-Rail 5 V HC, AHC, AC, LV-A, LV1T, LV4T



Mismatched logic levels



- Look more closely at the two levels to the right
 - Consider TTL output to CMOS input
 - The TTL High output could be 3.0V (>2.4V), but this will fall in the intermediate range for CMOS input (<3.5V)
 - So even though both are “5V Logic,” they may fail to work together
- This mismatch is even worse with differing voltage levels, ie. 3.3V and 5V
 - Devices called level shifters are used between the different logic levels

 

5-V TTL
 Standard TTL: ABT, AHCT, HCT, ACT, bipolar, LV1T, LV4T


5-V CMOS
 Rail-to-Rail 5 V HC, AHC, AC, LV-A, LV1T, LV4T



Unipolar Digital Signals



 - The voltage levels we just looked at are examples of unipolar signals
- In unipolar, low is assigned to 0 voltage, a.k.a ground. The high is assigned to the output voltage
- The idle state (when not actively transmitting) can either be High or Low






Bipolar Digital Signals



 - In some cases, you will see both positive and negative voltages used for a signal, called bipolar
- The signal may or may not return to 0V when idle







Single Ended Vs Differential



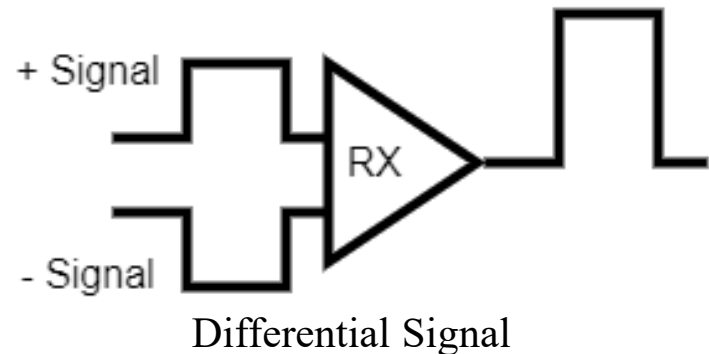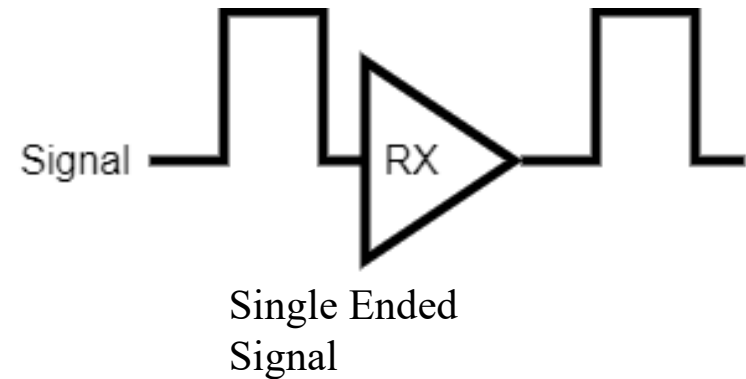- Signal can use a single wire and be measured compared to the device's 0V (GND)
 - This is called **Singled Ended**
 - This requires a common ground between the transmitting device and the receiving device
- An alternative is to use two lines and measure the difference
 - The signal is split and transmitted with opposite polarity, giving x2 the effective signal when received





Arduino Digital Signals




The Mega2560 Digital IOs have these characteristics

- Voltage Signals
- Unipolar
- Single Ended
- 5V TTL Logic

Digital Pins

- Except for the power pins, all of the pins on the Arduino headers can be used for basic digital input output
- Some of the pins have additional special functionality we will cover in later lectures
 - Pins A0-A15 can be used for analog input
 - Pins 0-1, 14-19 are for Serial Communication
 - Pins 20-21 I2C Communication
 - Pins 50-53 SPI Communication
 - Pins 2-13 can be used for analog output via a Technique Called Pulse Width Modulation (PWM)

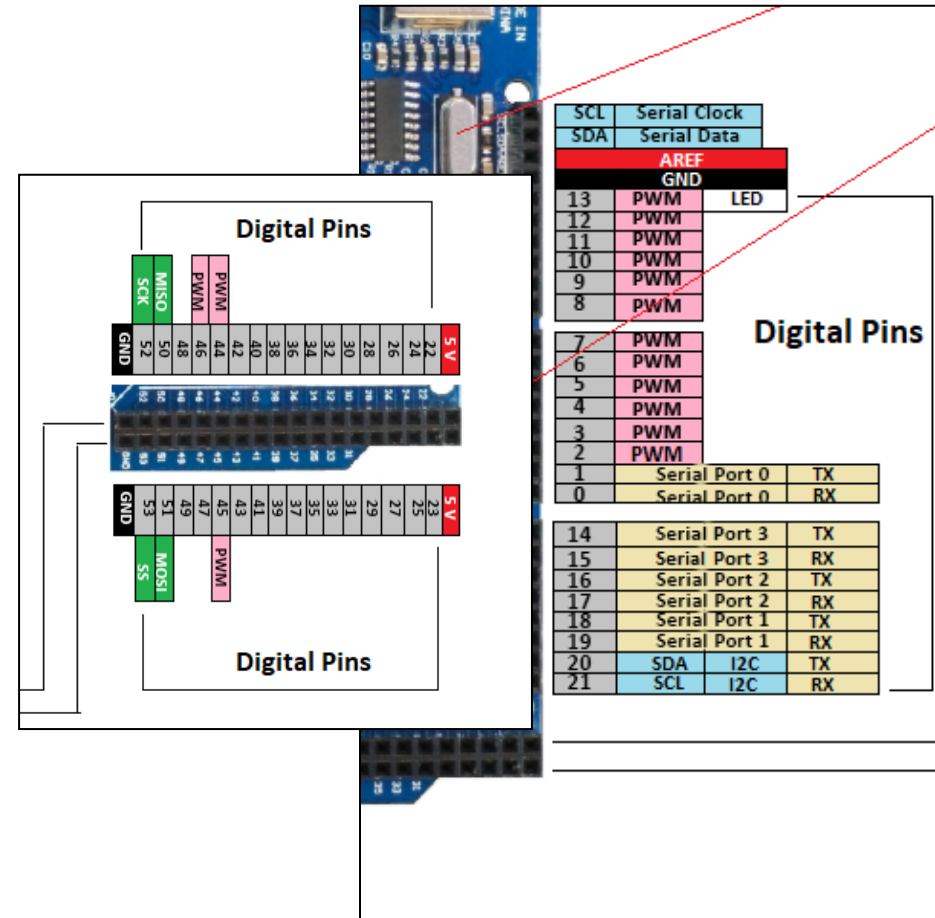




Digital Output Applications




To use a pin as an output, the Arduino controls the voltage of the output

 - Driving an LED with I/O pin as a current source.
- Driving an LED with I/O pin as a current sink.



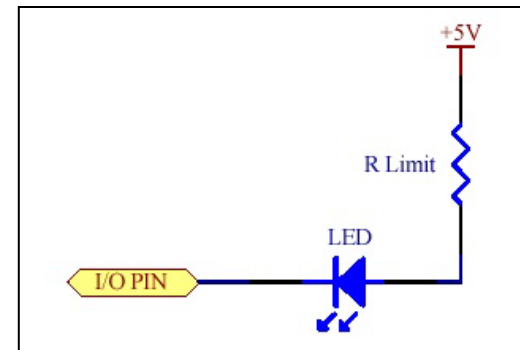HIGH pin turns LED on.
LOW pin turns LED off.




LOW pin turns LED on.
HIGH pin turns LED off.



Output Pin as a Current Source



 - In this case, the pin supplies the current to the load
- When a pin is HIGH, current flows from the pin through the load to GND
- When a pin is LOW, no potential difference between the pin and GND, so no current flows
- The Arduino can safely supply up to 40 mA




A current-limiting resistor may be needed in some applications to ensure the microcontroller is not damaged



I/O Pin as a Current Sink



- Sink in current sink refers to the pin's ability to receive current
- The current comes from some other source (External Power Supply, Arduino 5V pin)
- When pin is LOW, current flows from the +5V power supply through the load into I/O pin
- When the pin is HIGH, no potential difference between the pin and +5V, and no current flows
- The Arduino can safely sink 40 mA, the same as the source limit

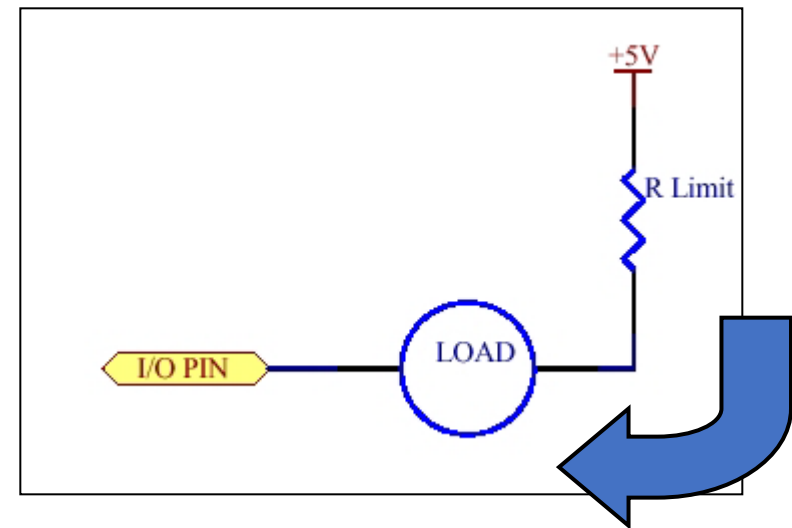


Again a current-limiting resistor may be needed in some applications to ensure the microcontroller is not damaged, especially if the external source is greater than 5V



Input Pins



 - Digital Inputs are even simpler
- The Arduino measures the voltage at the pin and returns a 1 for 5V and 0 for 0V
 - Similar to a multimeter, in voltage mode, the input pin will have a high resistance, so very little current will flow when the pin is being read





Floating Inputs



- So what happens if you try and read a pin that is not connected to anything
 - The unconnected pin is called “Floating”
- The pin will be in an unpredictable HIGH or LOW state depending on small charge or discharge paths on the PCB, Radio Frequency noise, temperature effects, etc.
- In most digital input applications, you want to remove the random effect and give a defined state by using a “Pull Up” or “Pull Down” resistor




Pull Up/ Pull Down




Pull Up resistors:

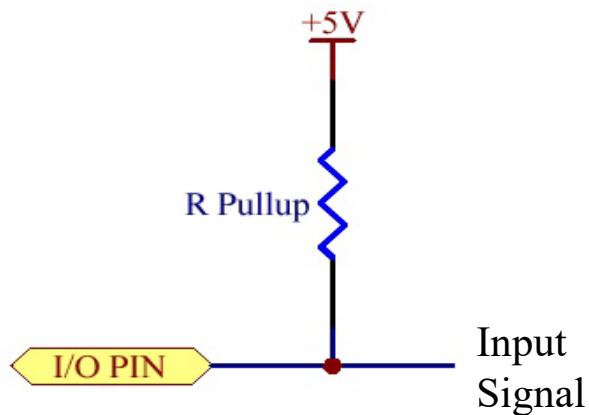- Connect the I/O Pin to +5V to “pull up” the voltage to the 1 value when the input is idle



Pull Down resistors:

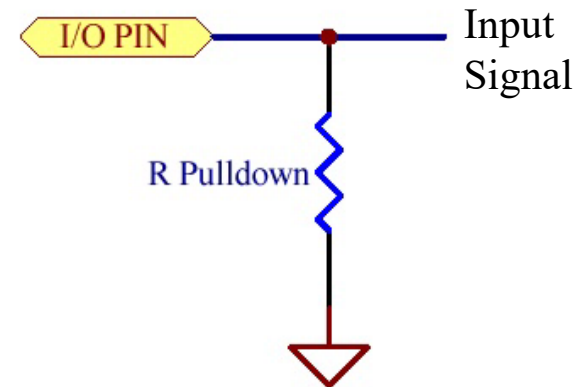- Connect the I/O Pin to 0V to “pull down” the voltage to the 0 value when the input is idle





Basic Digital I/O Functions



- We must set the pins as Input or Output
- The digital pins on the Arduino Mega are set to input as default (since this high resistance it is the safe state)
- To use digital pins we have 3 different functions
 - *pinMode(pin, mode)* sets the pin as an input or output
 - **INPUT** and **OUTPUT** are defined as variables so they can be used in mode
 - *digitalWrite(pin, value)* is used set a pin to 5V or 0V
 - **HIGH** and **LOW** are again defined variables so you can use them for value
 - *digitalRead(pin)* reads the pin and returns either a 1 (for 5V) or a 0 (for 0V)
 - For all, pin the number of the pin as labeled on the Arduino



Configuring Pins Examples



- Here is an example of setting pin 13 as an OUTPUT, and then “turns on” the pin for 1 second and then turns it off.

```
void setup()
{
  pinMode(13, OUTPUT);           // sets the digital pin 13 as output
}

void loop()
{
  digitalWrite(13, HIGH);       // sets the digital pin 13 on
  delay(1000);                  // waits for a second
  digitalWrite(13, LOW);        // sets the digital pin 13 off
  delay(1000);                  // waits for a second
}
```